

MULTIMEDIA



UNIVERSITY

STUDENT ID NO

--	--	--	--	--	--	--	--	--	--

MULTIMEDIA UNIVERSITY

SUPPLEMENTARY EXAMINATION

TRIMESTER 1, 2015 / 2016

PPH0135 - ELECTRICITY AND MAGNETISM
(Foundation in Engineering)


18 NOV 2015
9.00 AM – 11.00 AM
(2 HOURS)

INSTRUCTIONS TO STUDENT

1. This question paper consists of **FIVE (5)** printed pages excluding the cover page and appendices, with **FOUR (4)** questions.
 2. Answer **ALL** questions. The distribution of the marks for each question is given.
 3. Please write all your answers in the answer booklet provided.
-

QUESTION 1 (15 marks)

- a) **Figure Q1.1** shows a strip of silver with dimensions of $50.0\text{ mm} \times 20.0\text{ mm} \times 500.0\mu\text{m}$, is placed in a magnetic field ($B = 0.5\text{ T}$) directed perpendicular to the plane of the silver strip. A current $I = 12\text{ A}$ is sent down the strip as shown in the figure. If the electron density of silver is 5.86×10^{28} per m^3 , determine
- the drift velocity of electrons. (2 marks)
 - the magnitude and direction of the electric field in the strip. (2 marks)
 - the reading of the voltmeter V . (1 mark)
 - which side of the voltmeter is at the lower potential. (1 mark)

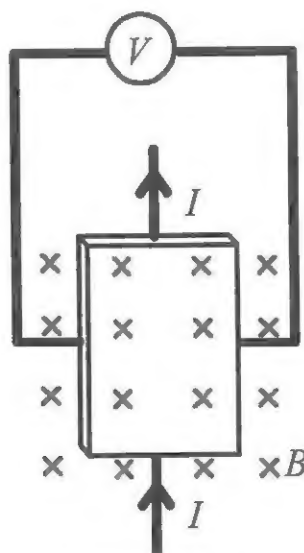**Figure Q1.1****Continued...**

- b) **Figure Q1.2** shows an electron moves in a circle of radius R in a uniform magnetic field B , directed out of the page.

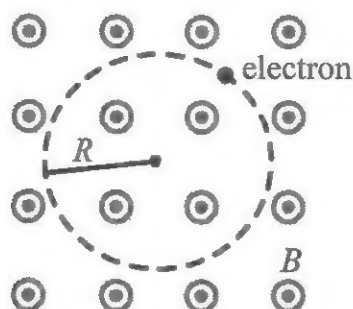


Figure Q1.2

- Does the electron move clockwise or counter clockwise?
(1 mark)
 - Derive an expression for the time taken for the electron to make one complete revolution.
(3 marks)
 - If $B = 0.2 \text{ T}$, determine the value in part (ii).
(1 mark)
- c) **Figure Q1.3** shows two conducting loops placed in the same plane. If switch S is closed,
- what is the direction of current flowing in loop 2? Explain.
(3 marks)
 - does the the current in loop 2 flow for only a short moment , or does it continue?
(1 mark)

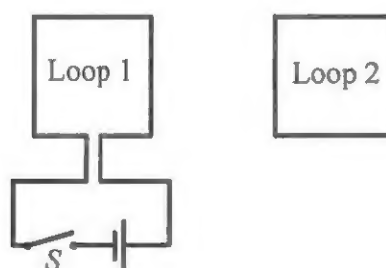
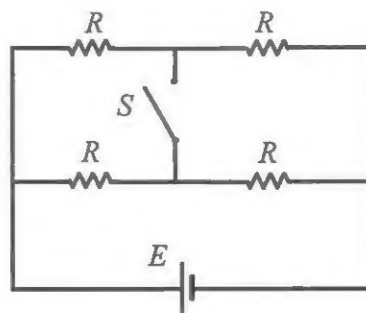


Figure Q1.3


Continued...

QUESTION 2 (15 marks)

- a) A battery is connected to a resistive load that has a resistance of $20.0\ \Omega$. A voltmeter across the battery reads $7.8\ \text{V}$ when the load is in place and $9.0\ \text{V}$ when the load is removed. Determine the internal resistance of the battery. (3 marks)
- b) Two tungsten wires, one with a diameter double of the other, have the same current flowing through them. If the drift speed of the thicker wire is v_1 , and the drift speed of the thinner wire is v_2 , calculate the ratio of the drift speeds. (3 marks)
- c) Four identical resistors are connected to a battery as shown in **Figure Q2.1**. When switch S is open, the current through the battery is I_0 . Calculate the current flows through the battery when the switch is closed. Give your answer in terms of I_0 . (3 marks)

**Figure Q2.1**

- d) Use Thevenin's theorem to find current through and voltage across R_1 in **Figure Q2.2**. Provide Thevenin equivalent circuit in your answer. (6 marks)

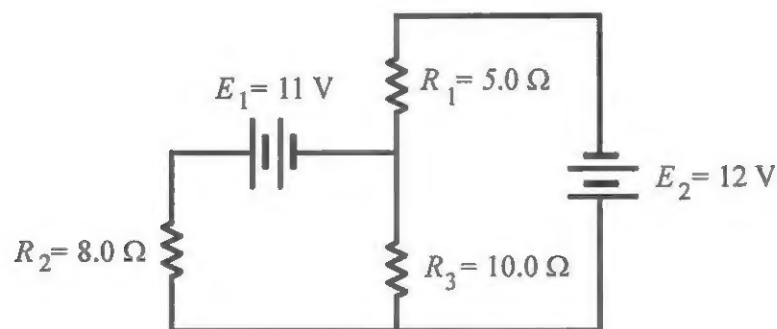**Figure Q2.2**

Continued...

QUESTION 3 (10 marks)

Figure Q3 shows a series RC circuit. The rms voltages across the resistor and the capacitor are the same.

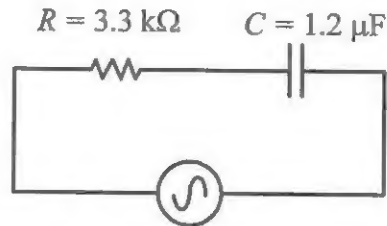


Figure Q3

- a) What is the frequency of the source? (2 marks)
- b) Write the rms voltages across the resistor and the capacitor in terms of the rms voltage of the source. (2 marks)
- c) What is the impedance of the circuit? (2 marks)
- d) What is the phase angle between the source voltage and current? Which leads? (2 marks)
- e) Draw a phasor diagram for the circuit. (2 marks)

QUESTION 4 (10 marks)

- a) **Figure Q4.1** shows a diagram of unbiased *pn* junction in equilibrium. The shaded area represents depletion region.

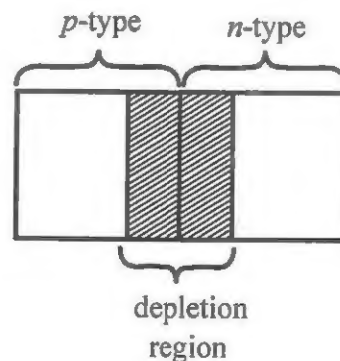


Figure Q4.1

Continued...

- i. What is the net charge of the pn junction? (1 mark)
 - ii. What is the net charge of the p -type? (1 mark)
 - iii. What is the net charge of the n -type? (1 mark)
 - iv. Does a pn junction have a capacitance behavior associated to it? Explain. (2 marks)
- a) Find the magnitude of I_B , I_E and I_C in **Figure Q4.2**, given that $\alpha_{dc} = 0.98$. Assume that the transistor is of germanium (Ge) type. (5 marks)

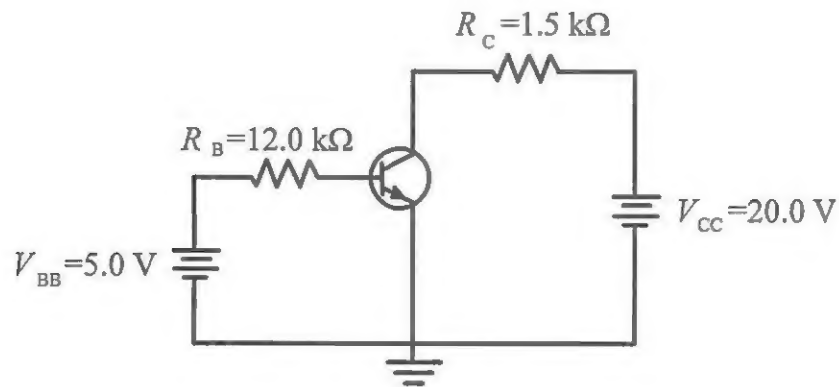


Figure Q4.2

Continued...

APPENDIX 1

Physical Constants

Quantity	Symbol	Value
Electron mass	m_e	$9.11 \times 10^{-31} \text{ kg}$
Proton mass,	m_p	$1.67 \times 10^{-27} \text{ kg}$
Elementary charge	e	$1.602 \times 10^{-19} \text{ C}$
Gravitational constant	G	$6.67 \times 10^{-11} \text{ N.m}^2/\text{kg}^2$
Gas constant	R	8.314 J/K.mol
Hydrogen ground state	E_0	-13.6 eV
Boltzmann's constant	k_B	$1.38 \times 10^{-23} \text{ J/K}$
Compton wavelength	λ_c	$2.426 \times 10^{-12} \text{ m}$
Planck's constant	h	$6.626 \times 10^{-34} \text{ J.s}$
Speed of light in vacuum	c	$3.0 \times 10^8 \text{ m/s}$
Rydberg constant	R_H	$1.097 \times 10^7 \text{ m}^{-1}$
Acceleration due to gravity,	g	9.81 m/s^2
Atomic mass unit (1u)	u	$1.66 \times 10^{-27} \text{ kg}$
Avogadro's number	N_A	$6.023 \times 10^{23} \text{ mol}^{-1}$
Threshold of intensity of hearing	I_0	$1.0 \times 10^{-12} \text{ W/m}^2$
Coulomb constant	k	$8.988 \times 10^9 \text{ N.m}^2/\text{C}^2$
Permittivity of free space	ϵ_0/κ_0	$8.85 \times 10^{-12} \text{ C}^2/\text{N.m}^2$
Permeability of free space	μ_0	$4\pi \times 10^{-7} \text{ H/m}$

Energy equivalent of atomic mass unit:

One atomic mass unit (1.0 u) is equivalent to 931.5 MeV

Continued...

APPENDIX II

List of formulas

$$A_v = \frac{V_c}{V_b}$$

$$\alpha_{dc} = \frac{\beta_{dc}}{\beta_{dc} + 1}$$

$$\beta_{dc} = \frac{\alpha_{dc}}{1 - \alpha_{dc}}$$

$$B = \frac{\mu_0 I}{2\pi r}$$

$$B = \mu_0 n I$$

$$\xi = V + Ir$$

$$\xi = blv$$

$$\xi = -N \frac{\Delta\Phi}{\Delta t}$$

$$\xi = -L \frac{dI}{dt}$$

$$\xi = -M \frac{dI}{dt}$$

$$F = BIL \sin \theta$$

$$F = qvB \sin \theta$$

$$\frac{F}{\ell} = \frac{\mu_0 I_1 I_2}{2\pi d}$$

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$I_{tot} = \sqrt{I_R^2 + (I_L - I_C)^2}$$

$$I = neA(v_n + v_p)$$

$$I = nev_d A$$

$$I = I_{max} \sin \omega t$$

$$I_{rms} = \frac{I_{max}}{\sqrt{2}}$$

$$I_x = \left(\frac{R_T}{R_x} \right) I_T$$

$$L = \frac{N\Phi_B}{I}$$

$$L = \frac{\mu_0 N^2 A}{l}$$

$$M = \frac{N\Phi_B}{I}$$

$$M = \frac{\mu_0 N_1 N_2 A}{l}$$

$$P = IV = I^2 R = \frac{V^2}{R}$$

$$P_t = I_{rms} V_{rms} \cos \phi$$

$$P_r = V_{rms} I_{rms} \sin \phi$$

$$P_a = I_{rms}^2 Z$$

$$R = \frac{\rho L}{A}$$

$$R = R_0 [1 + \alpha(T - T_0)]$$

$$R_T = R_1 + R_2 + R_3 + \dots$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

$$r = \frac{mv}{Bq}$$

$$\tau = NBIA \sin \theta$$

$$U = \frac{1}{2} LI^2$$

$$U = \frac{1}{2} B^2 A \frac{l}{\mu_0}$$

$$V_H = Bvd$$

$$V = V_{max} \sin \omega t$$

$$V_{rms} = \frac{V_{max}}{\sqrt{2}}$$

$$V_x = \left(\frac{R_x}{R_T} \right) V_s$$

$$X_C = \frac{1}{2\pi f C}$$

$$X_L = 2\pi f L$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\oint B \cdot dl = \mu_0 I$$

$$d\mathbf{B} = \frac{\mu_0 I}{4\pi} \frac{d\ell \times \hat{r}}{r^2}$$

$$\Phi_B = BA \cos \theta$$

$$\cos \phi = \frac{R}{Z}$$

$$\tan \phi = \frac{X_L - X_C}{R}$$

End of Page